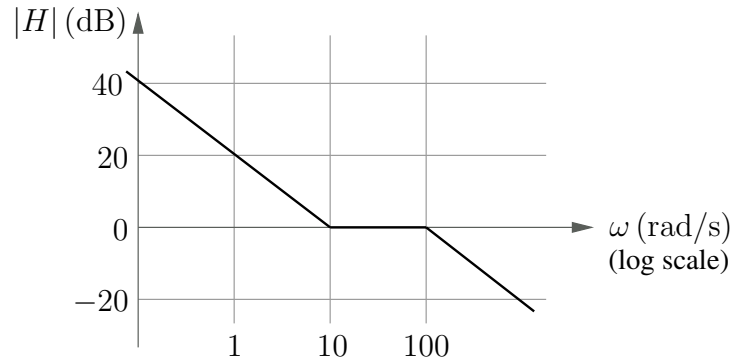


Basic Electronics


Instructor: M. B. Patil, IIT Bombay
Assignment for Week 8

1. Which of the following transfer functions corresponds to the magnitude Bode plot shown in the figure?




- (A) $\frac{10(s+100)}{s(s+10)}$ (B) $\frac{100(s+10)}{s(s+100)}$ (C) $\frac{10s}{(s+10)(s+100)}$ (D) $\frac{100(1+0.1s)}{(1+0.01s)}$
2. Consider the transfer function, $\frac{50s}{(s+10)(s+100)}$. What is the phase obtained using the Bode approximation at $\omega = 10 \text{ rad/s}$?
(A) 55° (B) 40° (C) 45° (D) 35°
3. For the transfer function of Q-2, what is the exact phase (i.e., without the Bode approximation) at $\omega = 10 \text{ rad/s}$?
(A) 39° (B) 44° (C) 34° (D) 52°
4. For the transfer function of Q-2, what is the phase obtained using the Bode approximation at $\omega = 100 \text{ rad/s}$?
(A) -60° (B) -35° (C) -24° (D) -45°
5. For the transfer function, $H(s) = \frac{200s}{1+0.01s}$, what is the phase obtained using the Bode approximation at $\omega = 500 \text{ rad/s}$?
(A) 16.2° (B) 11.3° (C) 13.5° (D) 15.5°

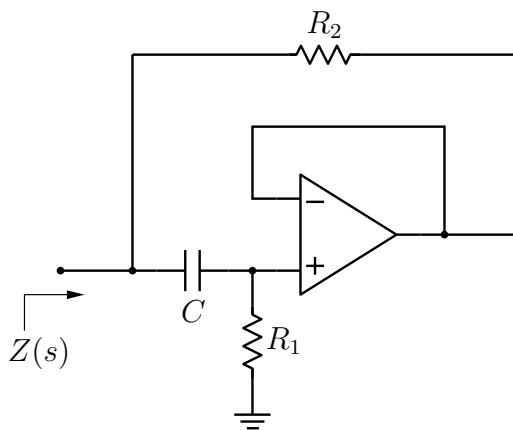6. The impedance $Z(s)$ in the figure is given by




- (A) $\frac{R_1}{1 + sR_1C}$ (B) $R_2 \frac{1 + sR_1C}{1 + sR_2C}$ (C) $\frac{R_1}{1 + sR_2C}$ (D) $\frac{1 + sR_2C}{1 + sR_1C}$

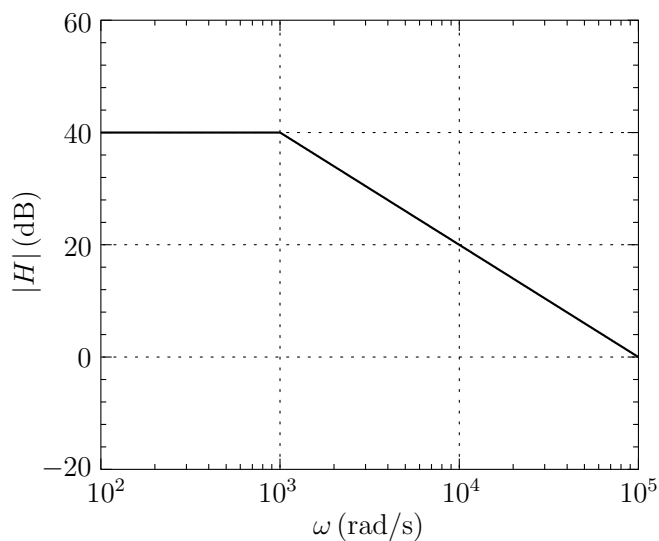
7. Which of the following graphs shows the correct Bode magnitude plot for the transfer function $H(s) = 10^2 \frac{1 + s/10^3}{1 + s/10^5}$?




(A)

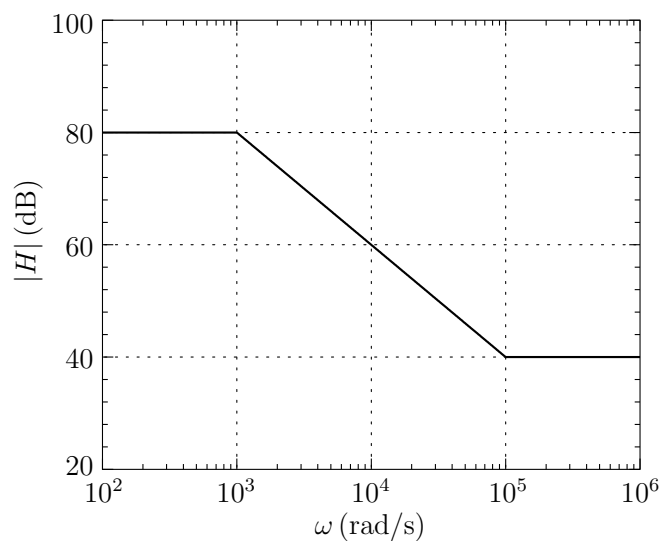

(B)

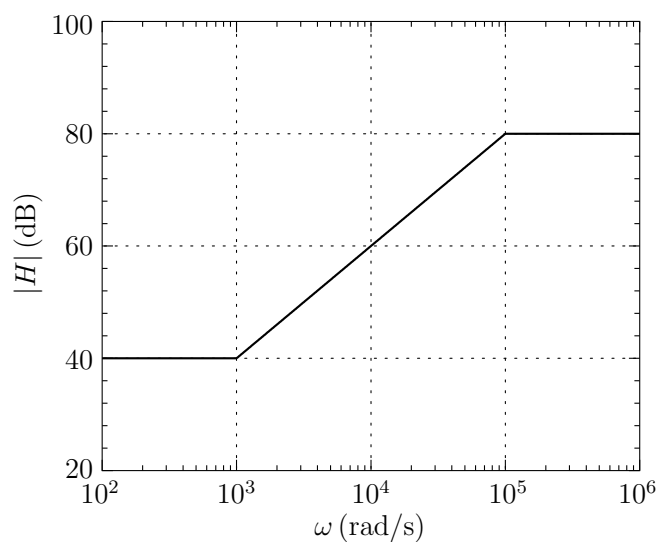


(C)

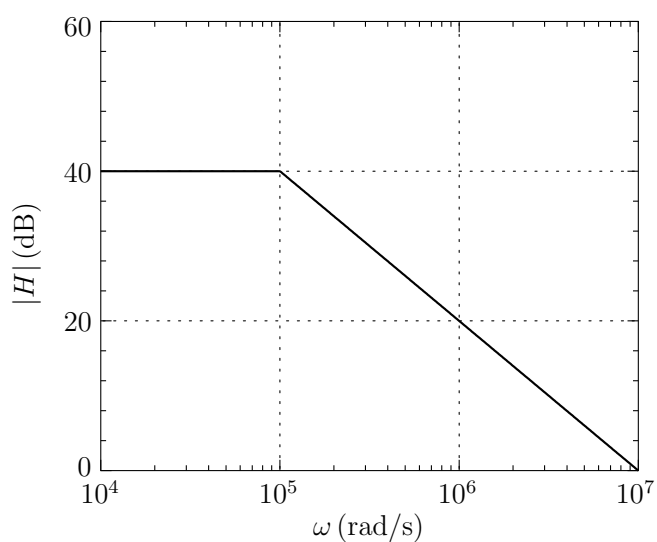


(D)

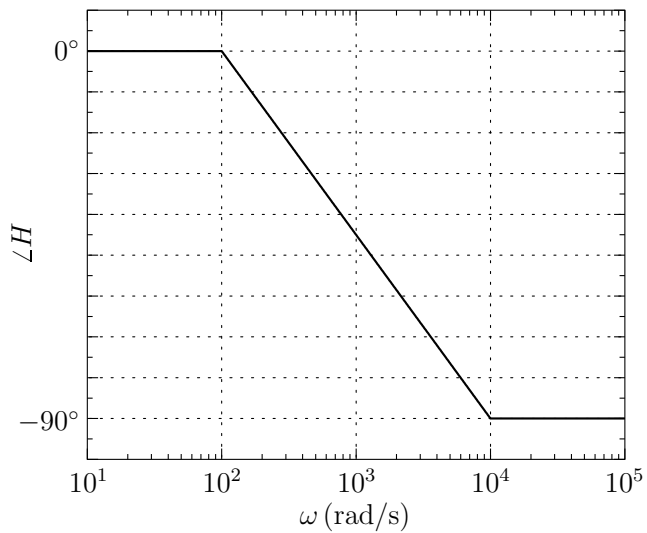
8. Which of the following graphs shows the correct Bode phase plot for the transfer function $H(s) = 10^2 \frac{1 + s/10^3}{1 + s/10^5}$?




(A)

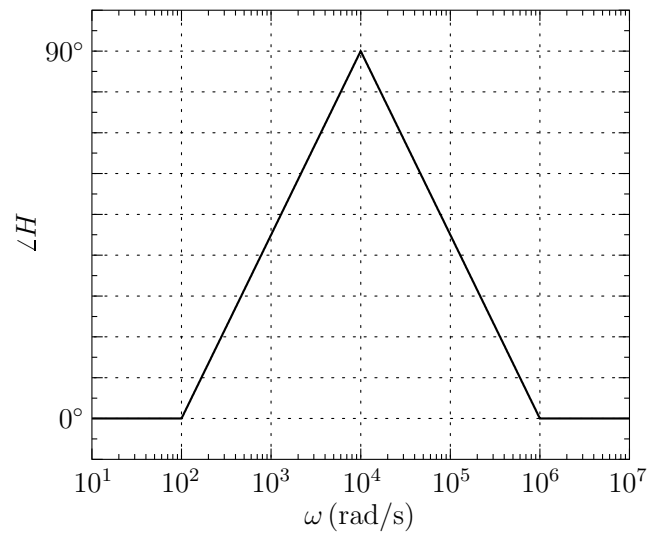

(B)

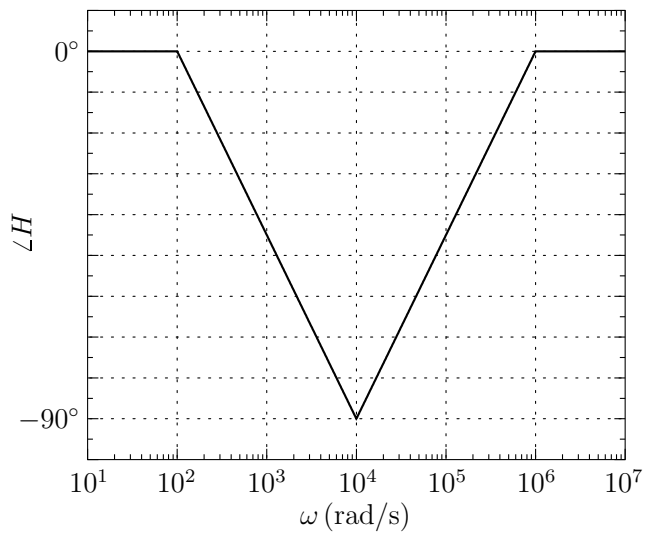


(C)

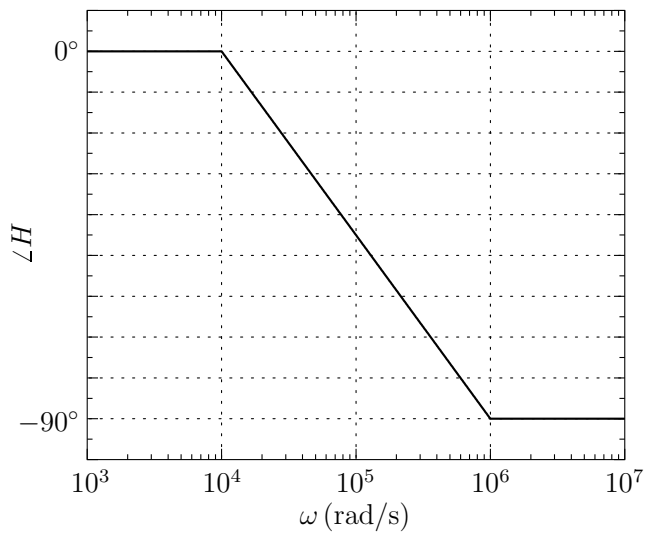


(D)

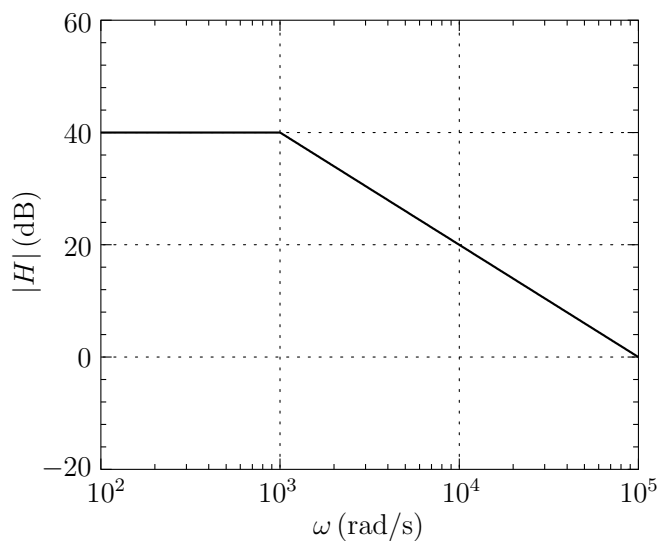
9. Which of the following graphs shows the correct Bode magnitude plot for the transfer function $H(s) = 10^4 \frac{1 + s/10^5}{1 + s/10^3}$?




(A)

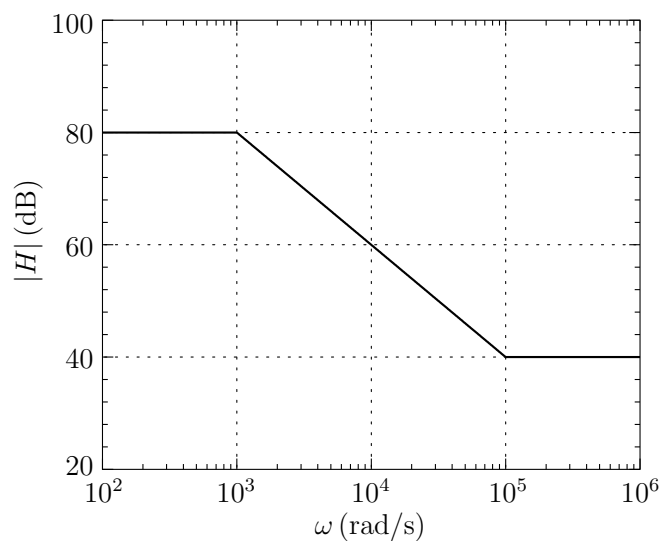

(B)

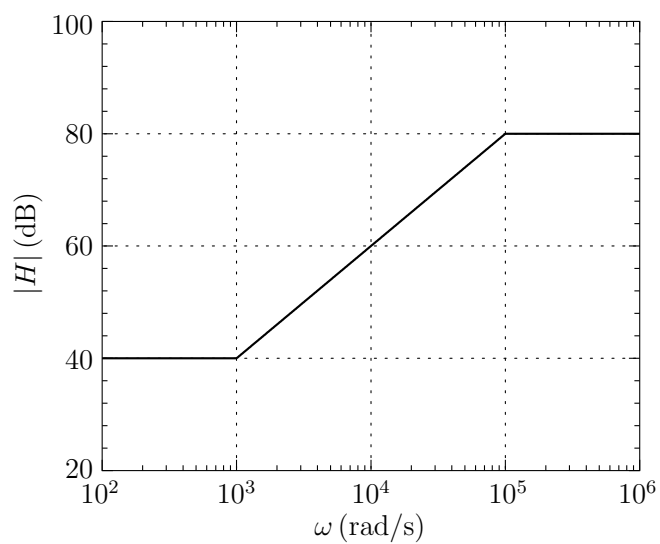


(C)

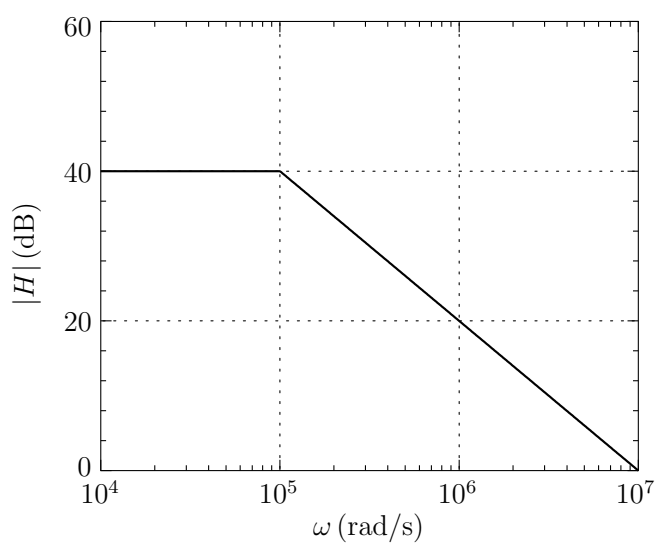


(D)

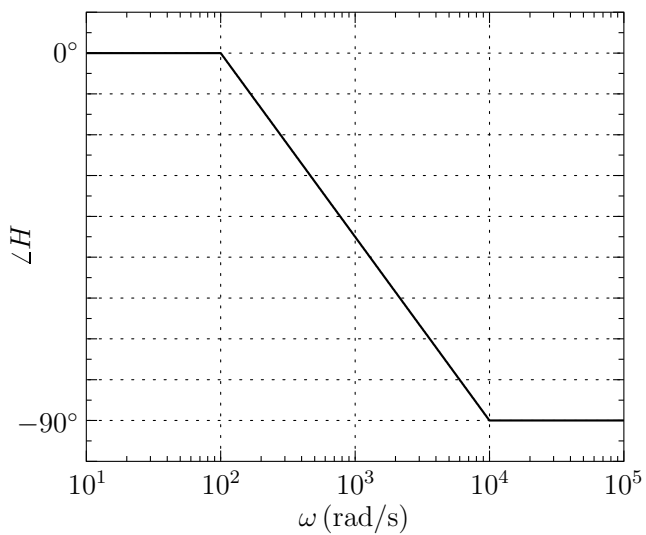
10. Which of the following graphs shows the correct Bode phase plot for the transfer function $H(s) = 10^4 \frac{1 + s/10^5}{1 + s/10^3}$?




(A)

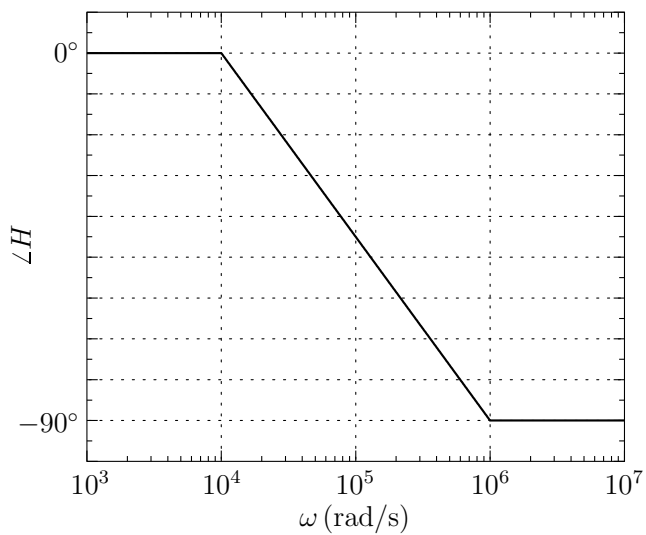

(B)


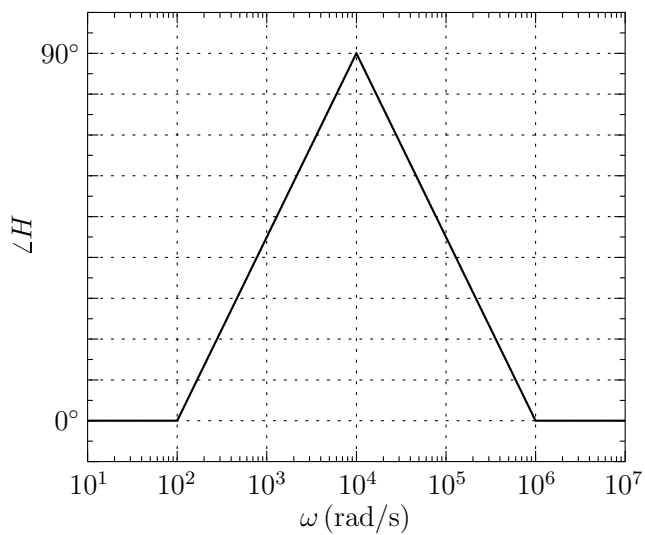


(C)

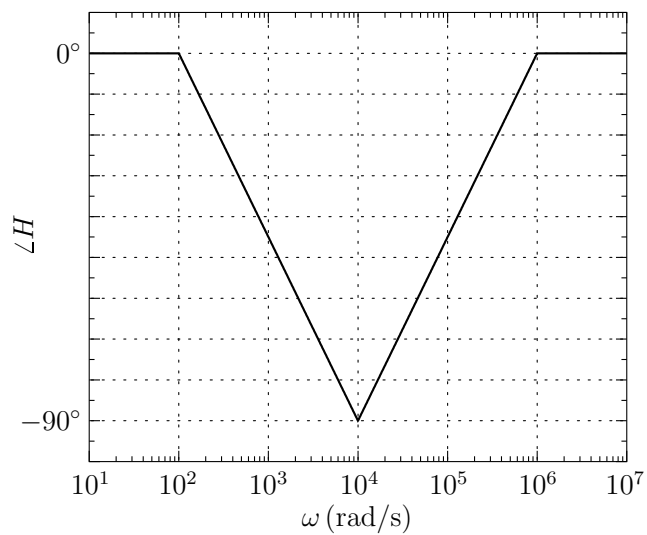


(D)

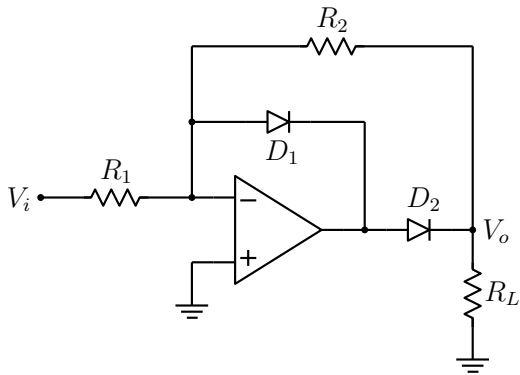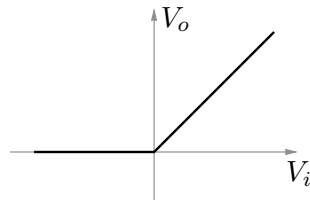
11. Which of the following circuits will produce the V_o versus V_i relationship shown in the figure?




(A)

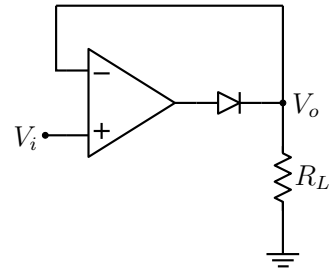

(B)


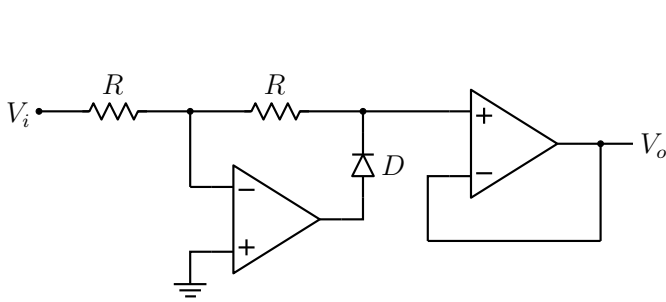


(C)

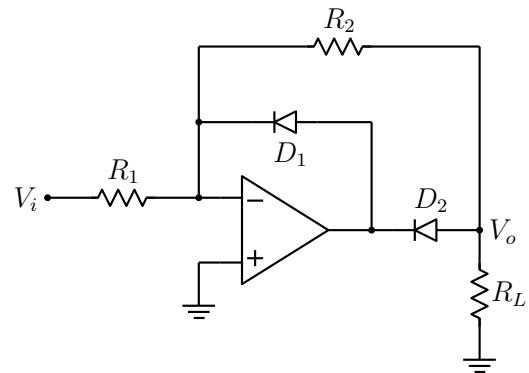


(D)

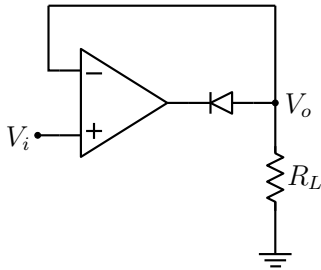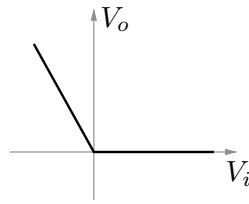
12. Which of the following circuits will produce the V_o versus V_i relationship shown in the figure?




(A)

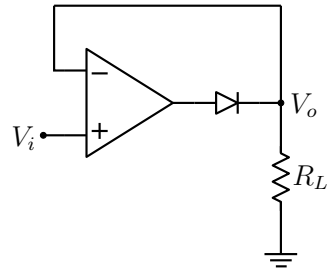

(B)


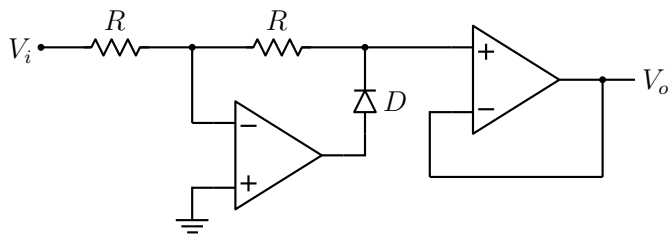


(C)

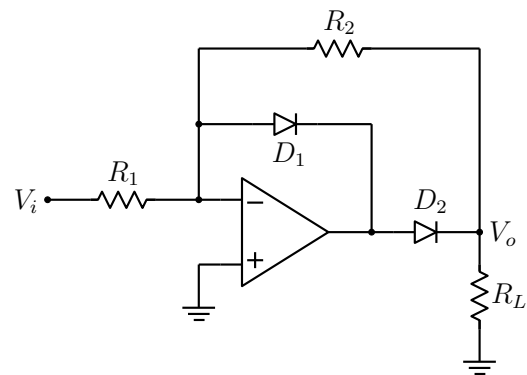


(D)

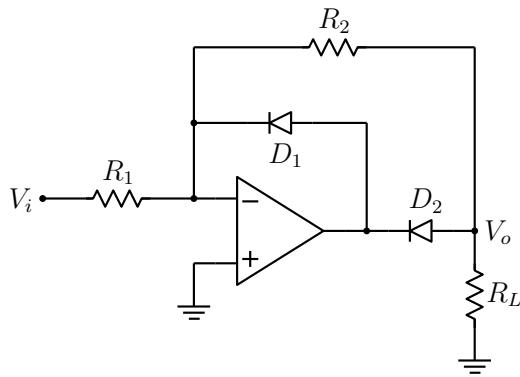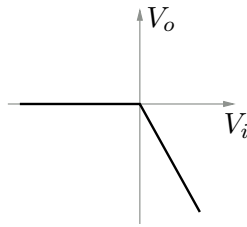
13. Which of the following circuits will produce the V_o versus V_i relationship shown in the figure?




(A)

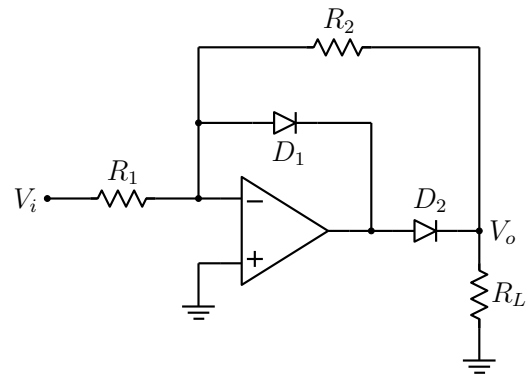

(B)


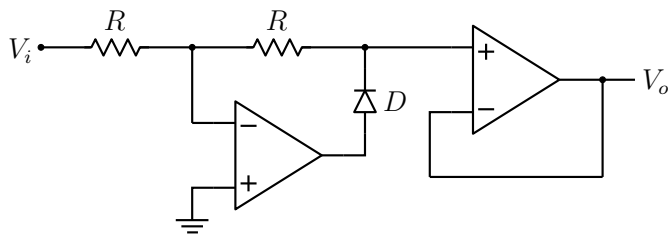


(C)

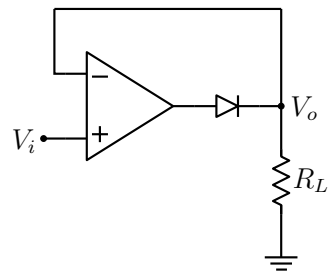


(D)

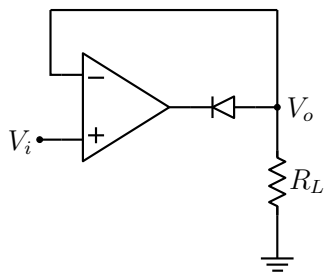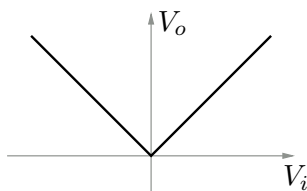
14. Which of the following circuits will produce the V_o versus V_i relationship shown in the figure?




(A)

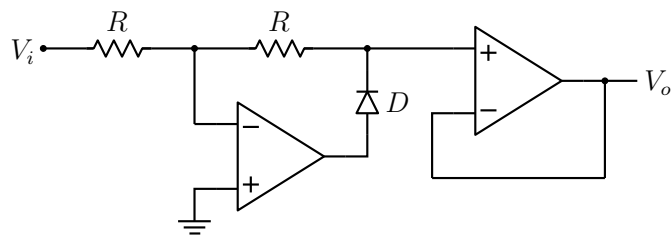

(B)


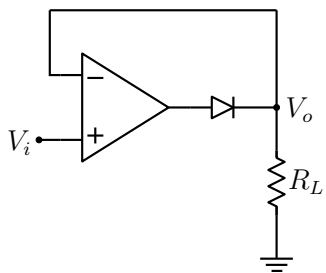


(C)

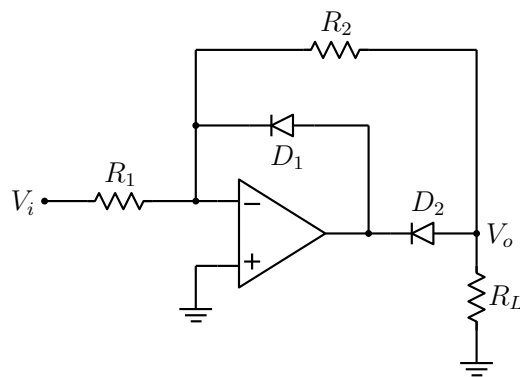


(D)

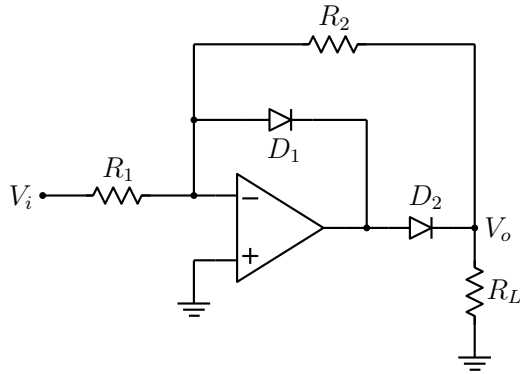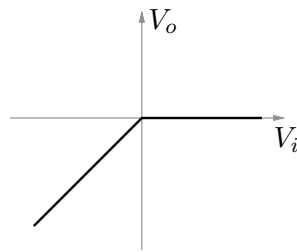
15. Which of the following circuits will produce the V_o versus V_i relationship shown in the figure?




(A)

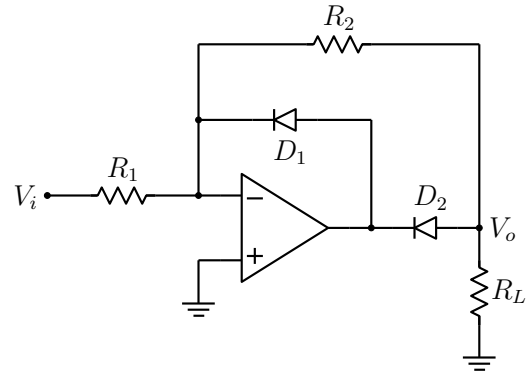

(B)

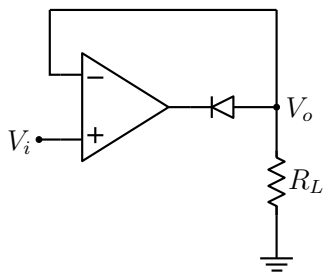

(C)

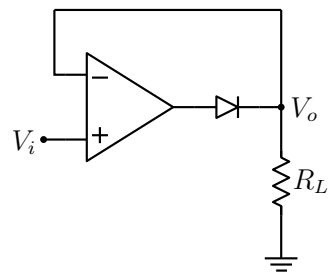

(D)